

S.B. Roll No.....

DIGITAL ELECTRONICS

3rd Exam/ECE/ETV/ECE-II/CSE/Comp/IT/EEE/0620/May'19

Duration: 3Hrs.

M.Marks:75

SECTION-A

Q1. Fill in the blanks.

15x1=15

- Two's complement of 110101 is_____.
- Hexadecimal system uses digits from_____.
- Hamming code is a one type of _____ code.
- BCD stands for _____.
- Boolean rule $(A+B)(A+C)=$ _____
- Half adder is also known as _____.
- Flip flop is not a _____ circuit.
- Race around condition do not occur in _____ FF.
- Data is said to be in serial form if the bits are available _____
- Analog to digital conversion is _____ complex than digital to analog conversion.
- LCD consumes _____ power than LED display.
- RAM stands for_____.
- A _____ signal varies continuously with time.
- For decade counter no. of Flip-Flop required will be_____.
- A NAND gate acts as a _____ OR gate.

SECTION-B

Q2. Attempt any five questions.

5x6=30

- Explain the Laws related to Boolean algebra.
- What do you mean by BCD codes? Explain.
- Explain operation of seven segment display.
- Explain various characteristics of standard TTL family.
- Explain RAM and ROM.
- Differentiate between a multiplexer and a Demultiplexer.
- Write down the application of A/D and D/A converter.
- Explain briefly the functioning of a serial in parallel out shift register.

SECTION-C

Q3. Attempt any three questions.

3x10=30

- Explain the working and construction of dual slope ADC.
- Discuss the OR, AND, NOT, NAND, NOR gates with their symbols and truth tables.
- What is latch? Explain working principle of J-K master/slave flip flop and draw its truth table.
- Write short note on the following. **(any two)** i) Hamming Code ii) Parity iii) Ring counter
- Minimize and realize following logic functions using K-map
 $f(A, B, C, D) = \sum m(0, 1, 2, 5, 8, 9, 10)$