

S.B. Roll No.....

DIGITAL ELECTRONICS

3rd Exam/ECE/ETV/ECE-II/CSE/EEE/0620/SEP'2020

Duration: 1.15 Hrs.

M.Marks:25

SECTION-A

Q1. Attempt any three questions.

3x5=15

- Convert the following: i) $85.63_{10} = X_2$ ii) $300.45_{10} = (?)_8$
- Draw symbol and truth table of NAND gate.
- Define noise margin, propagation delay and figure of merit.
- List the difference between analog and a digital signal.
- Draw and explain asynchronous Mod-5 counter.
- What are shift registers? Give its types.
- Draw and explain 2:1 Multiplexer
- Draw and implement half adder.
- What are the applications of shift registers?

SECTION-B

Q2. Attempt any one question.

1x10=10

- Simplify the following K-map and draw logic circuit using gates.
 $F(A,B,C,D) = \sum(1,5,7,8,9,10, 11,14, 15)$
- Explain the working and construction of a successive approximation type of ADC.
- Draw and give truth table of JK flip-flop. What is race around condition in JK flip-flop? How it can be avoided.
- Write Short note on the following. a) decoder b) combination circuit c) parity