

**DIGITAL ELECTRONICS**

**3<sup>rd</sup> Exam/ECE/ETV/ECE-II/Comp/IT/CSc/EEE/0620/May'18**

**Duration: 3Hrs.**

**M.Marks:75**

**SECTION-A**

**Q1. Do as directed.**

**10x1.5=15**

- Radix of Hexadecimal number is \_\_\_\_\_.
- ASCII code is \_\_\_\_\_ bit code.
- IC 7402 is \_\_\_\_\_ gate.
- BCD stands for \_\_\_\_\_.
- The expression  $A+B$  represents \_\_\_\_\_ gate.
- 1011 is a valid BCD number. (T/F)
- 2's complement of 1101 is \_\_\_\_\_.
- CMOS stands for \_\_\_\_\_.
- 8:1 Multiplexer has \_\_\_\_\_ number of select lines.
- SSI stands for \_\_\_\_\_.

**SECTION-B**

**Q2. Attempt any five questions.**

**5x6=30**

- What are advantages of digital signal?
- Draw and explain Half Adder.
- Explain the working of 3 bit asynchronous counter.
- Explain Universal gates with diagrams.
- Define noise margin, propagation delay and fan-out.
- Describe Ring counter with timing diagram.
- Explain the function of JK flip flop?
- Explain dual slope A/D converter.

**SECTION-C**

**Q3. Attempt any three questions.**

**3x10=30**

- Draw symbol and truth table of various logic gates.
- Simplify the given K-map and draw logic circuit using gates:  
 $F(A,B,C,D) = \sum(0,3,6,7,9,13,14,15)$
- Draw and explain BCD to decimal decoder. Give its applications also.
- Describe the operation of Universal Shift Register.
- Draw and explain the Full Subtractor.